

Homework 9

1a. 1024 bits $n = 16$

$$\frac{1024 \text{ bits}}{16 \text{ bits per word}} = 64 \text{ words}$$

6:64 decoder needed

6 bits in address

1b. 1024 bits $n = 8$

$$\frac{1024 \text{ bits}}{8 \text{ bits per word}} = 128 \text{ words}$$

7:128 decoder needed

7 bits in address

1c. 1024 bits $n = 64$

$$\frac{1024 \text{ bits}}{64 \text{ bits per word}} = 16 \text{ words}$$

4:16 decoder needed

4 bits in address

2. Initial:

Data = 001010, $R_1 = 010110$, $R_2 = 111000$, $R_3 = 000001$

Clk Signal 1

$$S_1, S_0 = 11$$

$$R_1 = 000001, R_2 = 111000, R_3 = 000001$$

Clk Signal 2

$$S_1, S_0 = 10$$

$$R_1 = 000001, R_2 = 111000, R_3 = 111000$$

Clk Signal 3

$$S_1, S_0 = 01$$

$$R_1 = 000001, R_2 = 111000, R_3 = 111000$$

Clk Signal 4

$S_1 S_0 = 00$


$R_1 = 000001, R_2 = 001010, R_3 = 111000$

Clk Signal 5

$S_1 S_0 = 11$

$R_1 = 000001, R_2 = 001010, R_3 = 111000$

3a.

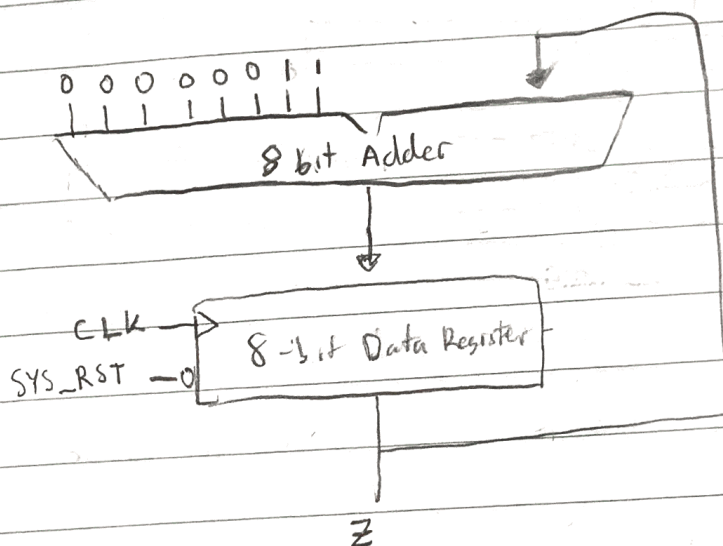

3b. After first rising clock edge - Output is 3.

After second rising clock edge - output is 6

After third rising clock edge - output is 9

After 85th rising clock edge - Output is 255


After 86th rising clock edge - Output is 2.

$$\begin{array}{r} 11111111 \\ 11111111 \\ 00000011 \\ \hline 100000010 \end{array}$$


3c

If I had a simple binary up counter with a smaller adder and smaller data storage register, I would have a two bit up counter and however many smaller adders and smaller data storage registers connected together to make one 8 bit adder and 8 bit data storage.

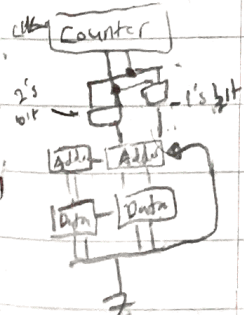
The carry out one adder would be the carry in for another adder. The Qn of data register will be the input for another register. The adders will only add when both 1's of the 2-bit counter are 1's then it would add 3 to adders.



4. 2:1 Mux using tri state driver

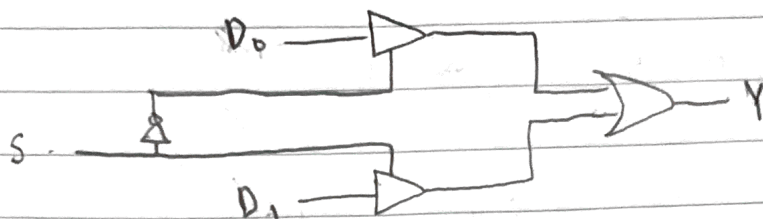

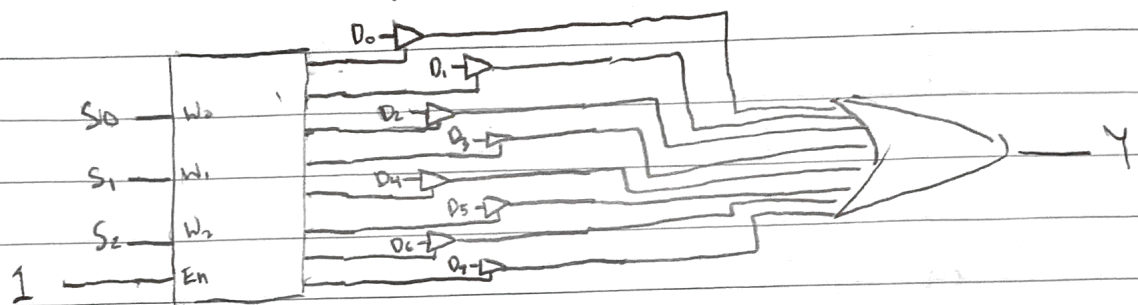8:1 MUX using 3:8 decoder and tri-state drivers



5a. 1001 0011 Even number of 1's, so no error

5b. 1001 1110 Odd number of 1's (5 1's),
Therefore there is a bit error.

All possible words

- 1001 1100	- 1000 1110	- 1011 1110
- 1001 1010	- 0001 1110	- 1101 1110
- 1001 0110	- 1001 1111	
- 1011 1110		

5c. 0010 1100 Odder number of 1's (3 1's)

Therefore, there is a bit error

Possible Words

- 0010 1101	- 0010 0100	- 0110 1100
- 0010 1110	- 0011 1100	- 1010 1100
- 0010 1000	- 0000 1100	

5d. 01010101 Even number of 1's, so no error

6. 1100 1100 PT D3 D2 D1 P4 D0 P2 P1

$$C1: P1 \oplus D0 \oplus P1 \oplus D3 = 0 \oplus 1 \oplus 0 \oplus 1 = 0$$

$$C2: P2 \oplus D0 \oplus P2 \oplus D3 = 0 \oplus 1 \oplus 0 \oplus 1 = 0$$

$$C4: P4 \oplus D1 \oplus D2 \oplus D3 = 1 \oplus 0 \oplus 0 \oplus 1 = 0$$

$$CT: PT \oplus D3 \oplus P2 \oplus D1 \oplus P4 \oplus D0 \oplus P2 \oplus P1 = \\ = 1 \oplus 1 \oplus 0 \oplus 0 \oplus 1 \oplus 1 \oplus 0 \oplus 0 = 0$$

$$CT = 0$$

$$C4C2C1 = 000$$

Number of bit errors = 0

Correct 8-bit word = 1100 1100

Correct 4 bit data word = 1001

0011 0010 PT D3 D2 D1 P4 D0 P2 P1

$$C1: 0 \oplus 0 \oplus 1 \oplus 0 = 1$$

$$C2: 1 \oplus 0 \oplus 1 \oplus 0 = 0$$

$$C4: 0 \oplus 1 \oplus 1 \oplus 0 = 0$$

$$CT: 0 \oplus 0 \oplus 1 \oplus 1 \oplus 0 \oplus 0 \oplus 1 \oplus 0 = 1$$

$$CT = 1$$

$$C4C2C1 = 001$$

Number of bit errors = 1

Correct 8 bit word = 0011 0011

Correct 4 bit word = 0110

1011 1010

PT D3 D2 D1 P4 D0 P2 P1

$$C1 = P1 \oplus D0 \oplus D1 \oplus D3 = 0 \oplus 0 \oplus 1 \oplus 0 = 1$$

$$C2 = P2 \oplus D0 \oplus D2 \oplus D3 = 1 \oplus 0 \oplus 1 \oplus 0 = 0$$

$$C4 = P4 \oplus D1 \oplus D2 \oplus D3 = 1 \oplus 1 \oplus 1 \oplus 0 = 1$$

$$CT = PT \oplus D3 \oplus D2 \oplus D1 \oplus P4 \oplus D0 \oplus P2 \oplus P1 = 1$$

$$CT = 1$$

$$C4C2C1 = 101$$

Number of bit errors = 1

Correct 8 bit word = 10101010

Correct 4 bit word = 0100

0010 0010

PT D3 D2 D1 P4 D0 P2 P1

$$C1 = 0 \oplus 0 \oplus 0 \oplus 0 = 0$$

$$C2 = 1 \oplus 0 \oplus 1 \oplus 0 = 0$$

$$C4 = 0 \oplus 0 \oplus 1 \oplus 0 = 1$$

$$CT = 0 \oplus 0 \oplus 1 \oplus 0 \oplus 0 \oplus 0 \oplus 1 \oplus 0 = 0$$

$$CT = 0$$

$$C4C2C1 = 100$$

Number of bit errors = 2

Correct 8 bit word = _____

Don't know since we

Correct 4 bit word = _____

don't know where the
2 bit errors are.