

II. PRE-LAB

- Be sure you understand 2's complement representation of signed numbers. See Appendix A. The 4-bit adder can be used for adding or subtracting since $(-B)$ represented in 2's complement form can be added to A to get $A-B = A+(-B)$.


The bit operations for addition are the **same for both** unsigned addition and signed addition using 2's complement representation. This is why 2's complement representation is so widely used. The bit pattern result is the same for both, but the **interpretation of the value of the bits will be different for signed and unsigned numbers**. (See Appendix A).

Fill in the table below for your adder Y inputs and carry-in input for each of the four operations listed. The operations are specified by $p1$ and $p0$ when $p3 = p2 = 0$. The first entry has already been completed for you.

Op-Select Input	Adder 4-bit X inputs	Adder 4-bit Y inputs	Adder Carry-in	Operation	Notes
$p3\ p2\ p1\ p0$	$a3\ a2\ a1\ a0$	$b3\ b2\ b1\ b0$			
0 0 0 0	$a3\ a2\ a1\ a0$	$b3\ b2\ b1\ b0$	0	$R=A+B$	Add
0 0 0 1	$a3\ a2\ a1\ a0$	$b3\ b2\ b1\ b0$	1	$R=A+B+1$	Add and Increment
0 0 1 0	$a3\ a2\ a1\ a0$	$b3' b2' b1' b0'$	0	$R=A-B-1$	Subtract and Decrement
0 0 1 1	$a3\ a2\ a1\ a0$	$b3' b2' b1' b0'$	1	$R=A-B$	Subtract

The *myadder4* component from the previous lab (Lab 5) will be used to perform the ALU's addition. The ALU A input will be connected to the adder X input, and the adder S output will be the ALU R output. The adder Y input and carry-in to the adder will depend on which operation is selected, as defined by the table above.

 - Use a 4-bit adder symbol, a 4-bit wide 2:1 MUX, and other logic components as needed to design this first part of the arithmetic unit. Based on your table, use a 4-bit wide 2:1 MUX to produce the Y adder input with $p1$ as the select. Add logic for the adder carry in input. Draw the schematic for your design.



- Modify your design to include the next four operations shown in the problem statement table when $p2=1$. A second 4-bit wide 2:1 MUX with $p2$ as the select can be used to create the inputs to the MUX used in the previous step. Draw a schematic for your design.
- Write a hierarchical Verilog module *myALU4* which uses *myadder4*. The ALU inputs will be P , A , B , and $C0$. The outputs will be R , $C4$, V , and Z . It will perform the eight operations described in the problem statement.
 - Add logic to make the carry input to the adder.

A hand-drawn schematic diagram of a circuit. A central rectangular box contains the labels 'X', 'Y', 'CO', 'V', and 'S'. To the left of the box is a label 'C4'. Below the box is a label '4'. To the right of the box is a label 'CO'. Above the box, there are two labels '4' and '4' connected to a horizontal line. This line leads to a component labeled 'P1' which is connected to a component labeled 'B'. To the right of 'B' is a label 'P'. Below the box, there is a label 'Z' connected to a vertical line. This vertical line is connected to a label 'V' and then to a label 'R' at the bottom right. There is also a label 'C4' on the far left connected to the bottom line.

[illegible]

Since we don't know how to do 4c, I'm going to call the output of the two muxes (input to Y) wire 2.

5) - p_0 controls whether there is a carry in or not for the adder.

- p_1 controls whether something is being added to or subtracted from A. So it controls the operation (add/subtract) being performed on A.
- p_2 controls the B input. If p_2 is 0, then B is being added or subtracted from the equation. If p_2 is 1, then B input is not apart of the operation being done to A input.

6) Step 1: Set $P=0000$, $A=0010$, $B=0001$, $CO=0$

Outputs $R=0011$, $Z=0$, $V=0$, $C4=0$

- Test that the two Muxes are working, no carry in and that p operations are right

Step 2: Set $P=0001$, $A=0010$, $B=0001$, $CO=1$

Outputs $R=0100$, $Z=0$, $V=0$, $C4=0$

- Test Addition with increment and that carry in is working

Step 3: Set $P=0010$, $A=0010$, $B=0001$, $CO=0$

Outputs $R=0000$, $Z=1$, $V=0$, $C4=0$

- Test subtraction with decrement and that Z is working

Step 4: Set $P=0011$, $A=0010$, $B=0001$, $CO=1$

Outputs $R=0001$, $Z=0$, $V=0$, $C4=0$

- Test subtraction and that carry in of 1 is being done.