

Kendall Won
Matt Seminatore

COEN 21 Lab 4

In this lab, we are creating an adder for two-bit integers. It takes in the three inputs and a fourth selector input using multiplexers to select which functions to use. We made two function blocks for each output, and a multiplexer chose between them using the input A1. We used Shannon's expansion to design the functions. As a result, we created a circuit that added two numbers between 0-3 and added them to get a number from 0-6.

$$S0F0 = A0'B0 + A0B0'$$

$$S0F1 = A0'B0 + A0B0'$$


$$S1F0 = A0'B1 + B1B0' + A0B1'B0$$

$$S1F1 = A0'B1' + B1'B0' + A0B1B0$$

$$S2F0 = A0B1B0$$

$$S2F1 = B1 + A0B0$$

S0

 

S1

S1

$A_1 A_0$ $B_1 B_0$	00	01
00	0	0
01	0	1
11	1	0
10	1	1

$A_1 A_0$ $B_1 B_0$	11	10
00	1	1
01	0	1
11	1	0
10	0	0

$$f_{s1}(0, A_0, B_1, B_0) = A_1' A_0' B_1 + A_1' B_1 B_0' + A_1' A_0 B_1' B_0$$

$$f_{s1}(1, A_0, B_1, B_0) = A_1 A_0' B_1' + A_1 B_1' B_0' + A_1 A_0 B_1 B_0$$

S2



S2

$A_1 A_0$ $B_1 B_0$	00	01
00	0	0
01	0	0
11	0	1
10	0	0

$A_1 A_0$ $B_1 B_0$	11	10
00	0	0
01	1	0
11	1	1
10	1	1

$$f_{s2}(0, A_0, B_1, B_0) = A_1' A_0 B_1 B_0$$
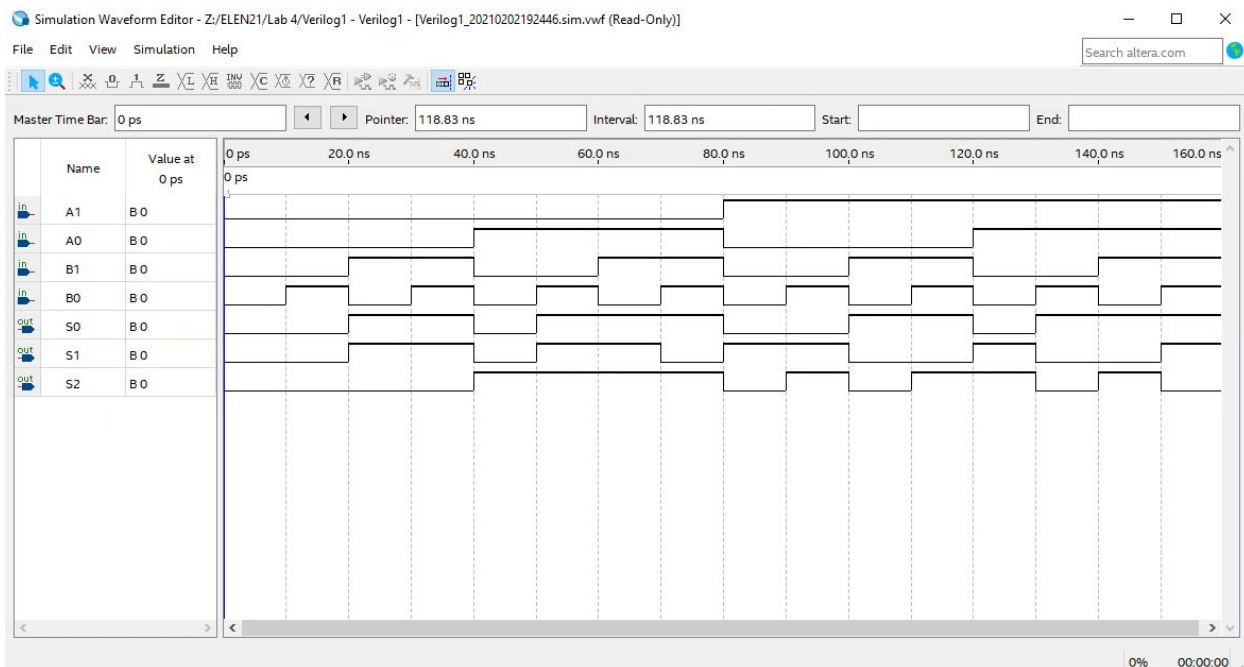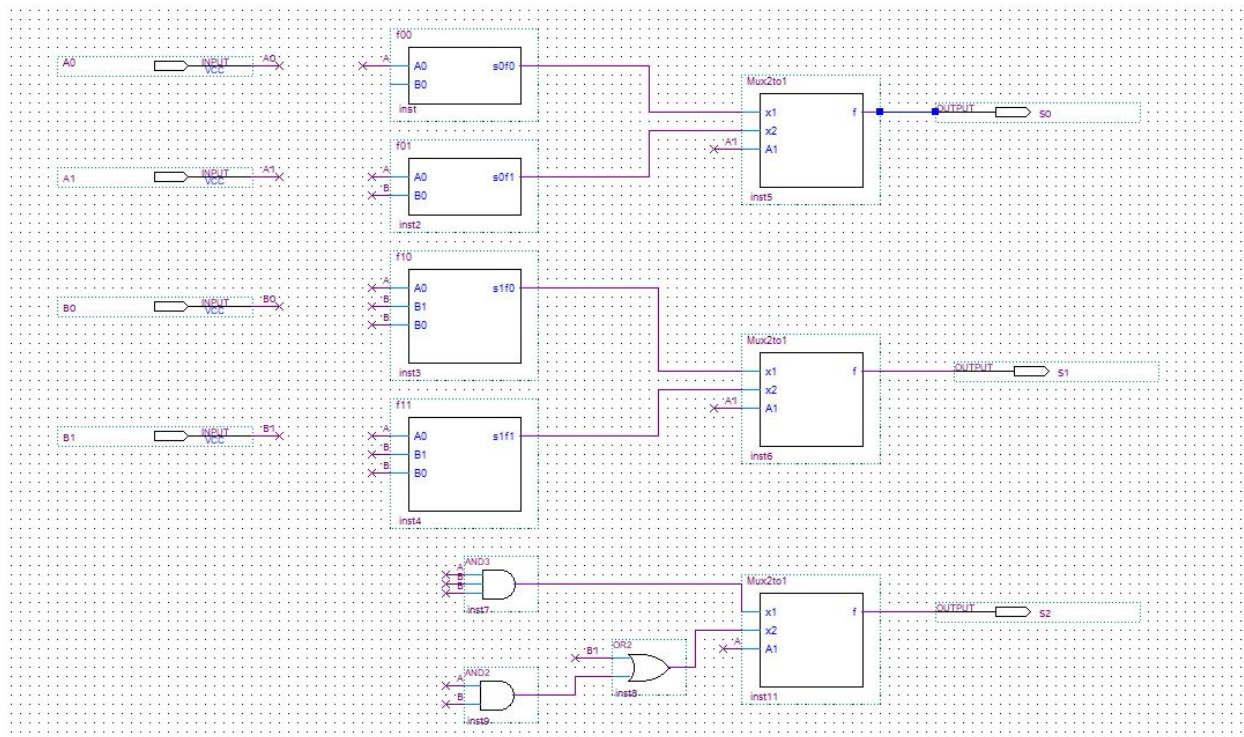
$$f_{s2}(1, A_0, B_1, B_0) = A_1 B_1 + A_1 A_0 B_0$$



```
module Mux2to1 (x1,x2,A1,f);
    input x1,x2,A1;
    output f;

    assign f= (~A1&x1)|(A1&x2);

endmodule
```

```
module f00 (A0,B0,s0f0);
    input A0,B0;
    output s0f0;

    assign s0f0=A0^B0;

endmodule
```

```
module f01 (A0,B0,s0f1);
    input A0,B0;
    output s0f1;

    assign s0f1=A0^B0;

endmodule
```

```
module f10(A0,B1,B0,s1f0);
    input A0,B1,B0;
    output s1f0;

    assign s1f0=(~A0 & B1)|(B1 & ~B0)|(A0 & ~B1 & B0);

endmodule
```

```
module f11(A0,B1,B0,s1f1);  
    input A0,B1,B0;  
    output s1f1;  
  
    assign s1f1=(~A0 & ~B1)|(~B1 & ~B0)|(A0 & B1 & B0);  
  
endmodule
```

Conclusion

In this lab, we learned how to implement Verilog designs and the usefulness of Verilog in organizing logical circuit schematics at higher levels of complexity. We didn't face any challenges with our Verilog or schematics. The only challenges we faced were small errors that required the TA's assistance to fix. For example, having to change the name of Waveform.vwf to Waveform4.vwf in the simulation settings.