


Homework 5

1a)

	ab	00	01	11	10
c	0	0	0	1	1
1	0	1	1	0	0

$$X = AC' + BC$$

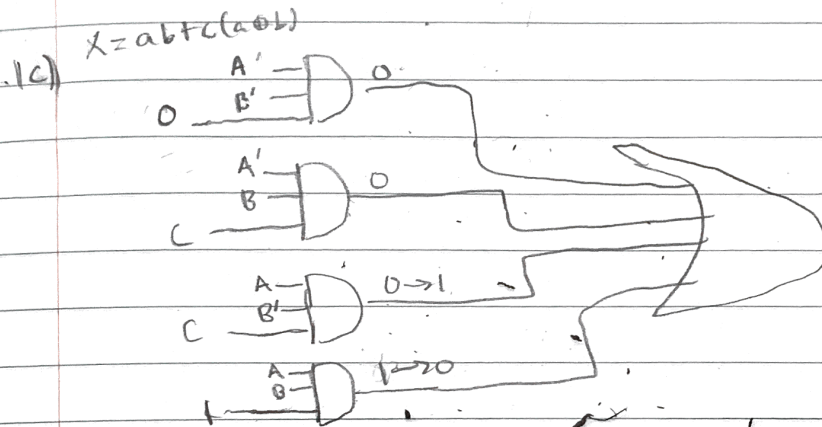If $A=B=1$
and C changes
there can be
a static 1 hazard
due to gate delays
and changing.



If B flips, it can
change the output to
zero for a moment between
gate delays before
settling back to
1

1d)

		$a'b'c'$
		$a'b'c$
		$a'bc'$
		$a'bc$
		$ab'c'$
		$ab'c$
		abc'
		abc

In a 3:8 decoder, there is a static
1 hazard between all minterms because
any change will change all to zero
but one will change to 1 after going
through gate delays within the decoder.

1b) $X = ab + c(a \oplus b)$

	ab	00	01	11	10
c	0	0	0	1	0
1	0	1	1	1	1

↑ ↑
static hazard

If a flips or b flips when the other
one equals 1, then they can
cause a static hazard, due
to gate delay.

Homework 5

due Wednesday 10 February 2021

1. For the following implementations of a three-input majority circuit, identify any static 1 hazards. For each static 1 hazard, specify the input values and the single input change that would cause the hazard to appear.
 - a. In a minimized SOP form
 - b. In the form of the carry out of the full adder: $c_{k+1} = a_k \cdot b_k + c_k \cdot (a_k \oplus b_k)$
 - c. Using a 4:1 Mux with two of the three inputs connected to the selects
 - d. Using a 3:8 decoder
2. Complete the timing diagram below for the circuit in Figure 5.4a, explicitly including the effect a delay of ΔT between a change in the input values and the response at the output. Each square has a duration of ΔT and the initial state is $Q_a=0$ and $Q_b=1$.


 
 
 




Figure 5.4 a from text

 3. Complete the timing diagram below for the circuit shown in Figure 5.10a. Do not explicitly show gate delays. Use the functional definition for the latch and flip-flop, and assume that the setup and hold requirements are satisfied.



← Figure 5.10a from text

  4. For the circuit in Figure 5.17a, complete the timing diagram below. Assume set-up and hold time requirements are met. Do not explicitly show propagation delays through the flip-flops.



5. Modify the circuit in Figure 5.17a to allow a synchronous clear option. If an input **ClearReg** is 1, all four flip-flops should be cleared on a rising clock edge. If the input **ClearReg** is 0 the circuit should function as it did before the modification.

