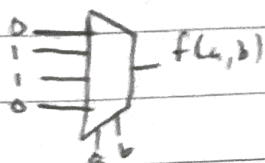


Homework 3

1a. 4:1 MUX $s_1 = a$ $s_0 = b$ $w_0 = 0$, $w_1 = 1$, $w_2 = 1$, $w_3 = 0$

$$f(a,b) = a'b + ab'$$

a	b	$f(a,b)$
0	0	0
0	1	1
1	0	1
1	1	0




a \ b	0	1
0	0	1
1	1	0

1b. 2:1 MUX $s = b$ $w_0 = a$ $w_1 = a'$

a	b	$f(a,b)$
0	0	0
0	1	1
1	0	1
1	1	0

$$f(a,b) = ab' + a'b$$

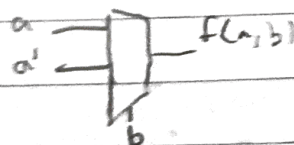


a \ b	0	1
0	0	1
1	1	0

1c. $f(a,b,c)$ 4:1 MUX $s_1 = b$ $s_0 = c$ $w_0 = 0$, $w_1 = c$, $w_2 = a$, $w_3 = 1$

a	b	c	$f(a,b,c)$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$$f(a,b,c) = ab'c + abc' + bc$$

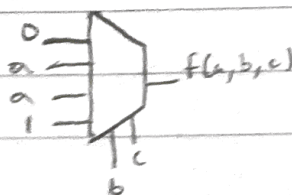


a \ b \ c	00	01	11	10
0	0	0	1	0
1	0	1	1	1

1d. $f(a,b,c)$ 2:1 MUX $s = c$ $w_0 = a'$ $w_1 = b$

a	b	c	$f(a,b,c)$
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

$$f(a,b,c) = a'c' + bc$$

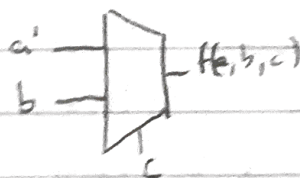


a \ b \ c	00	01	11	10
0	1	1	0	0
1	0	1	1	0

1e. $f(a,b,c)$ 2:1 MUX $s = a$ $w_0 = (b+c')$ $w_1 = (bc)$


a	b	c	$f(a,b,c)$
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

$$f(a,b,c) = a'(b+c') + abc$$

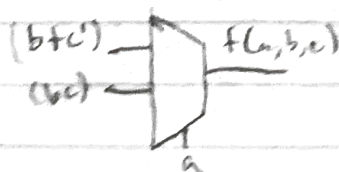

a \ b \ c	00	01	11	10
0	1	1	0	0
1	0	1	1	0

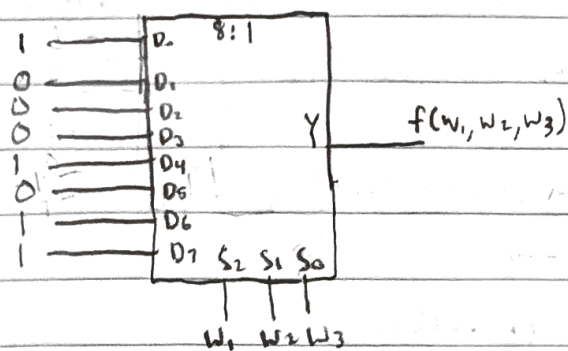2a. $f(w_1, w_2, w_3) = \sum m(0, 4, 6, 7)$




2b. $w_1 \quad w_2 \quad w_3 \quad | \quad f(w_1, w_2, w_3)$

0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

$f(0, w_2, w_3) = w_2' w_3'$

$f(1, w_2, w_3) = w_2' w_3' + w_2 w_3' + w_2 w_3$
 $= w_2 + w_3'$

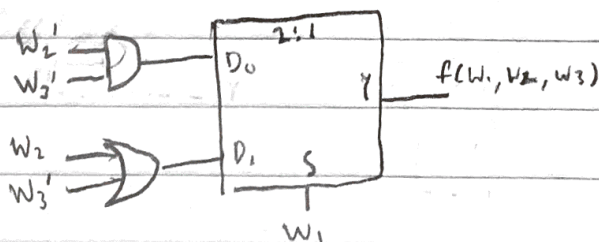$f(w_1, w_2, w_3) = w_1' \cdot w_2' w_3' + w_1 \cdot (w_2 + w_3')$
 $= w_1' w_2' w_3' + w_1 (w_2 + w_3')$




2c.

w_1	w_2	w_3	f
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

$f(w_1, 0, w_3) = w_1' w_3' + w_1 w_3' = w_3'$

$f(w_1, 1, w_3) = w_1 w_3' + w_1 w_3 = w_1$

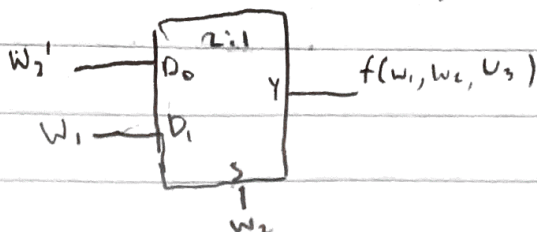$f(w_1, w_2, w_3) = w_2' \cdot w_3' + w_1 w_2$




2d.

w_1	w_2	w_3	f
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

$$f(w_1, w_2, 0) = w_1'w_2' + w_1w_2' + w_1w_2 = w_1 + w_2'$$

$$f(w_1, w_2, 1) = w_1w_2$$

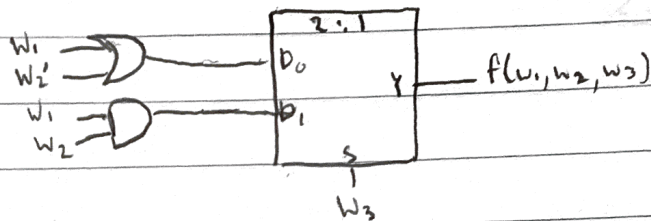
$$f(w_1, w_2, w_3) = w_3' \cdot (w_1 + w_2') + w_3 \cdot w_1w_2$$



- 2e.
- b: 2 gates, 1 multiplexer, 7 inputs
 - c: 0 gates, 1 multiplexer, 3 inputs
 - d: 2 gates, 1 multiplexer, 7 inputs

3a. $f(a, b, c) = (ab) \oplus (ac)$


a	b	c	$f(a, b, c)$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

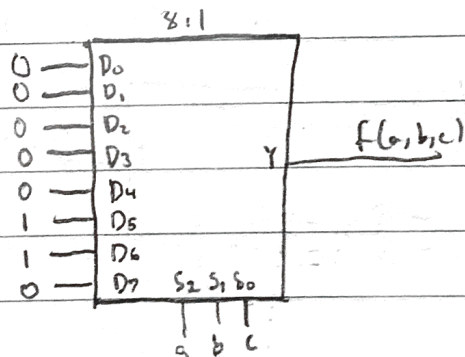

3b. $f(0, b, c) = 0$

$$f(1, b, c) = b'c + bc'$$

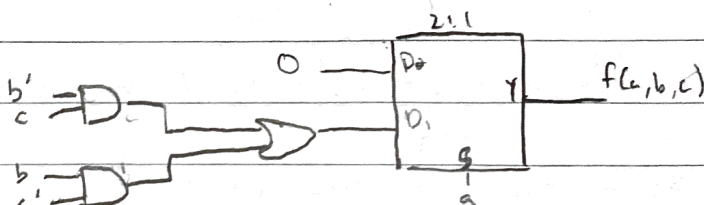
$$f(a, b, c) = a' \cdot 0 + a(b'c + bc')$$



3c. $f(a, 0, c) = ac$

$f(a, 1, c) = ac'$


$f(a, b, c) = ab'c + abc'$

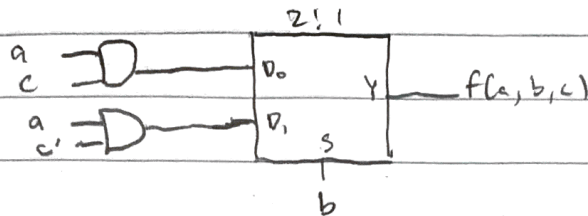

3d. $f(a, b, 0) = ab$

$f(a, b, 1) = ab'$

$f(a, b, c) = abc' + ab'c$

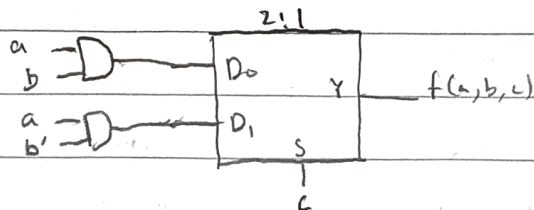


3e. b: 3 gates; 1 MUX, 8 inputs

c: 2 gates; 1 MUX, 7 inputs


d: 2 gates, 1 MUX, 7 inputs

4a.

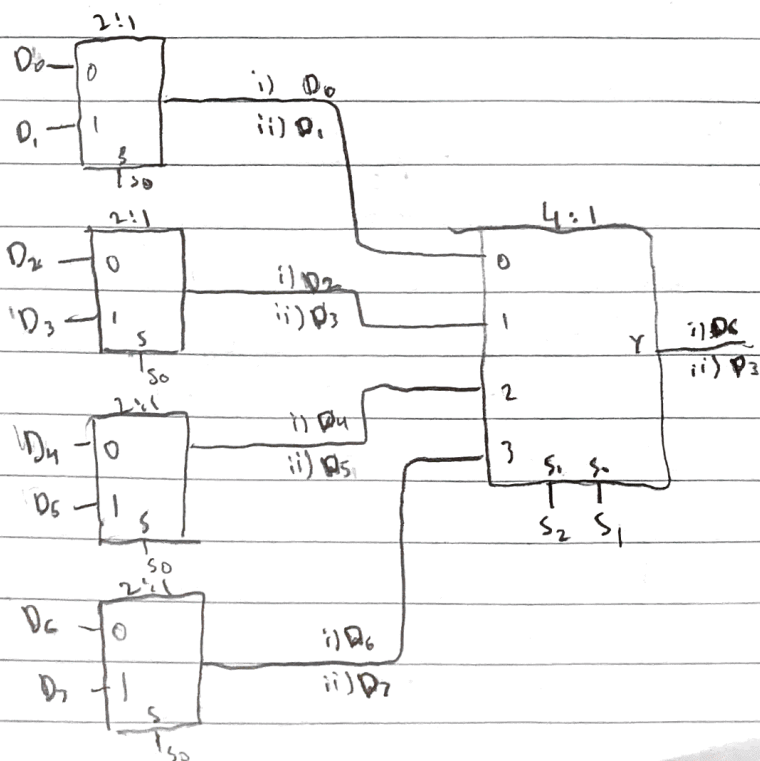

i) $s_2 s_1 s_0 = 110 \rightarrow D_6$

ii) $s_2 s_1 s_0 = 011 \rightarrow D_3$

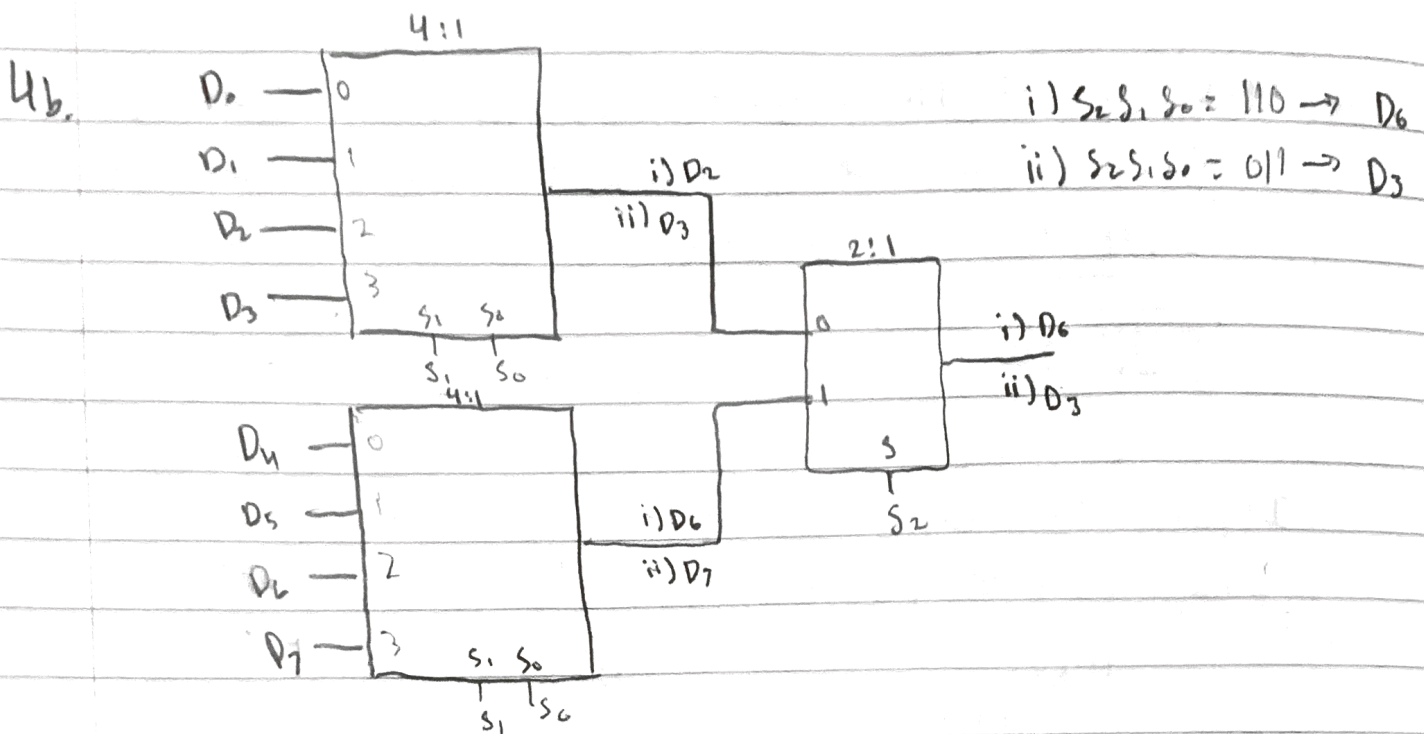


4c. 4b & 4c both get the same final output.


The number of inputs in the each systems is different. For 2:1 MUX to one 4:1 MUX has 12 inputs, while two 4:1 MUX to 2:1 MUX only has 10 inputs. The two 4:1 MUX to 2:1 MUX is better because less inputs which makes it easier to find the output of the system.

5a.

E_n	W_1	W_0	Y_0	Y_1	Y_2	Y_3
0	x	x	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

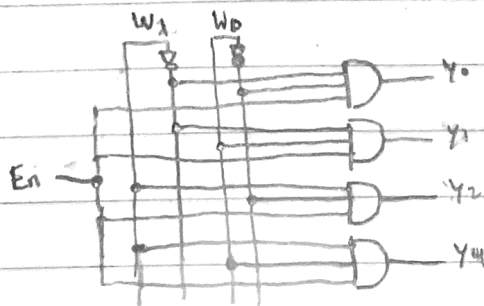


5b.

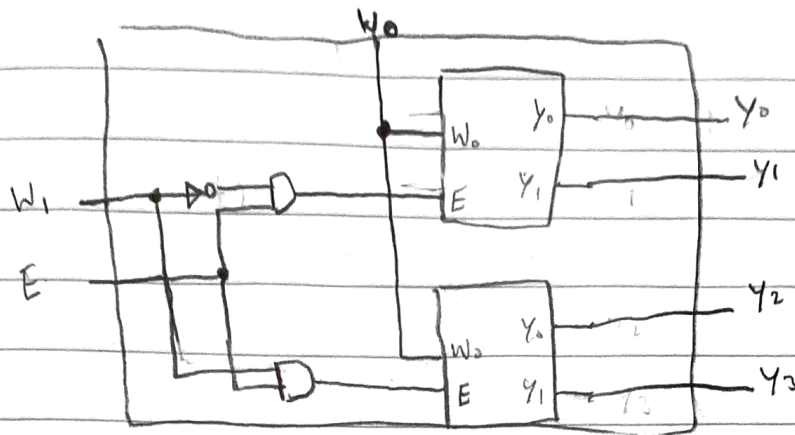


i) Two 1:2 decoders are needed

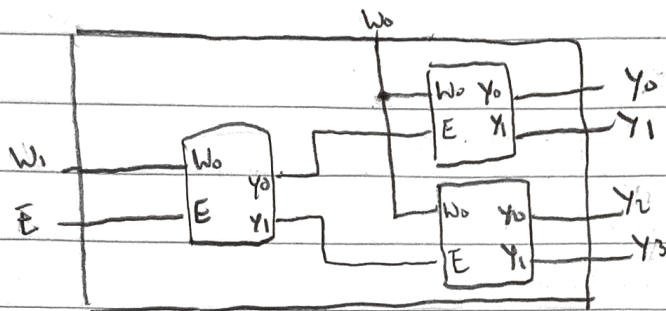ii) It is possible to create a 2:4 decoder using only 1:2 decoders. You will have three 1:2 decoders. The input for the enable for the second and third 1:2 decoders will be the output of the first 1:2 decoder.



5c.

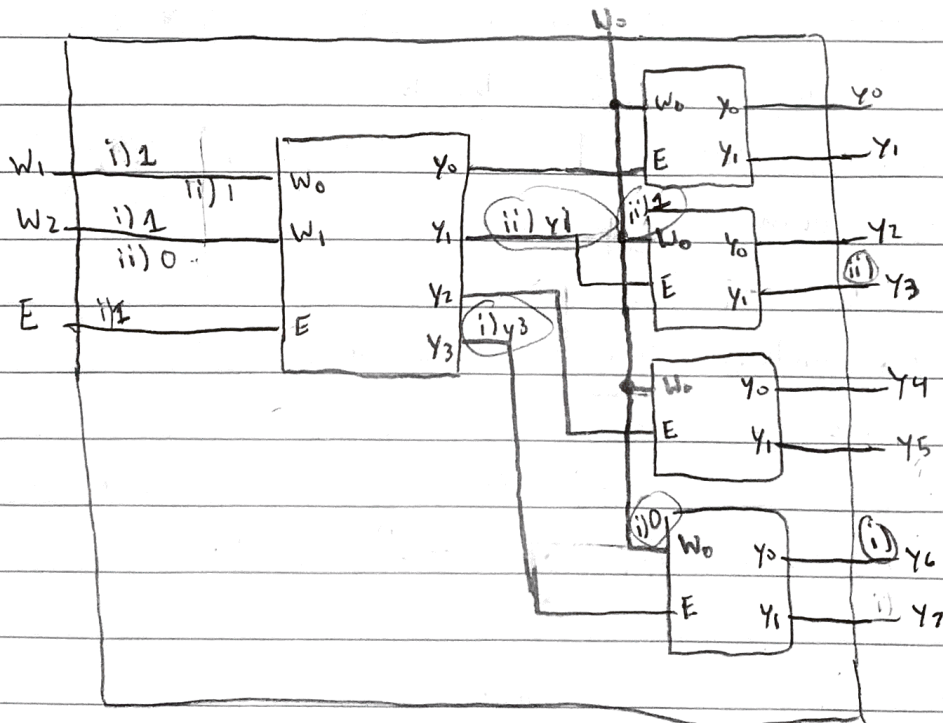

i) $W_2 W_1 W_0 = 110 \rightarrow Y_6$

ii) $W_2 W_1 W_0 = 011 \rightarrow Y_3$

6a. $(101011)_2$

5 4 3 2 1 0
32 16 8 4 2 1

$$1 \times 32 + 0 \times 16 + 1 \times 8 + 0 \times 4 + 1 \times 2 + 1 \times 1 =$$

$$32 + 8 + 2 + 1 = (43)_{10}$$

6b. $(0101011)_2$

$$\begin{array}{r} 6 \ 5 \ 4 \ 3 \ 2 \ 1 \ 0 \\ 64 \ 32 \ 16 \ 8 \ 4 \ 2 \ 1 \end{array}$$

$$0 \times 64 + 1 \times 32 + 0 \times 16 + 1 \times 8 + 0 \times 4 + 1 \times 2 + 1 \times 1$$

$$32 + 8 + 2 = (43)_{10}$$

6c. $(0011111)_2$

$$\begin{array}{r} 6 \ 5 \ 4 \ 3 \ 2 \ 1 \ 0 \\ 64 \ 32 \ 16 \ 8 \ 4 \ 2 \ 1 \end{array}$$

$$0 \times 64 + 0 \times 32 + 1 \times 16 + 1 \times 8 + 1 \times 4 + 1 \times 2 + 1 \times 1$$

$$16 + 8 + 4 + 2 + 1 = (31)_{10}$$

6d. $(111100)_2$

$$\begin{array}{r} 5 \ 4 \ 3 \ 2 \ 1 \ 0 \\ 32 \ 16 \ 8 \ 4 \ 2 \ 1 \end{array}$$

$$1 \times 32 + 1 \times 16 + 1 \times 8 + 1 \times 4 + 0 \times 2 + 0 \times 1 = 32 + 16 + 8 + 4 = (60)_{10}$$

6e. $(111110)_2$

$$\begin{array}{r} 5 \ 4 \ 3 \ 2 \ 1 \ 0 \\ 32 \ 16 \ 8 \ 4 \ 2 \ 1 \end{array}$$

$$1 \times 32 + 1 \times 16 + 1 \times 8 + 1 \times 4 + 1 \times 2 + 0 \times 1 = 32 + 16 + 8 + 4 + 2 = (62)_{10}$$

7a. $(101011)_2$

$$\begin{array}{r} 5 \ 4 \ 3 \ 2 \ 1 \ 0 \\ 32 \ 16 \ 8 \ 4 \ 2 \ 1 \end{array}$$

$$-32 + 8 + 2 + 1 = (-21)_{10}$$

7b. $(0101011)_2$

$$\begin{array}{r} 6 \ 5 \ 4 \ 3 \ 2 \ 1 \ 0 \\ 64 \ 32 \ 16 \ 8 \ 4 \ 2 \ 1 \end{array}$$

$$32 + 8 + 2 + 1 = (43)_{10}$$

$$7c. (0011111)_2$$

6 5 4 3 2 1 0

64 32 16 8 4 2 1

$$16 + 8 + 4 + 2 + 1 = (31)_{10}$$

$$7d. (111100)_2$$

5 4 3 2 1 0

32 16 8 4 2 1

$$-32 + 16 + 8 + 4 = (-4)_{10}$$

$$7e. (111110)_2$$

5 4 3 2 1 0

32 16 8 4 2 1

$$-32 + 16 + 8 + 4 + 2 = (-2)_{10}$$