

Name: Kendall Won

Partner: Haohan Li


### COEN 21 Lab #1

1. Was the schematic you created in your pre-lab correct or not? If it was incorrect, in what way was it incorrect? What do you think led you to your incorrect schematic?

The schematic that I created in my pre-lab was correct. My partner's pre-lab schematic was also correct.

2. If your pre-lab schematic was incorrect, provide a corrected schematic

My Schematic:

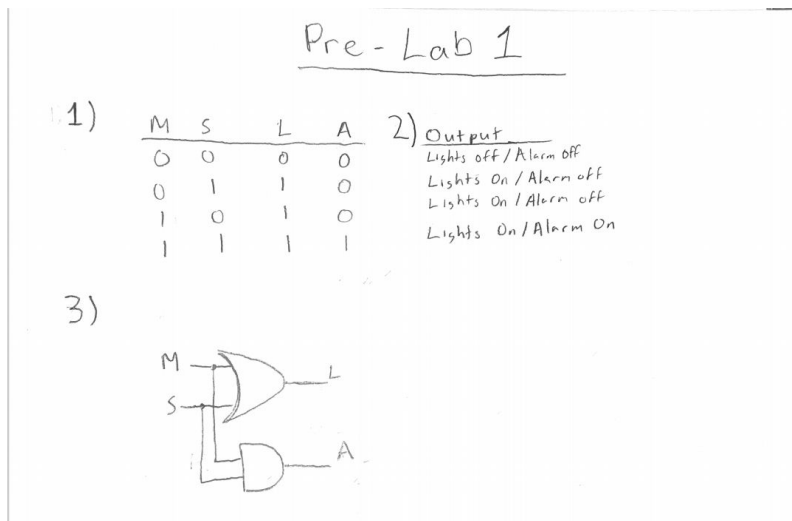

Partner's Schematic:

